
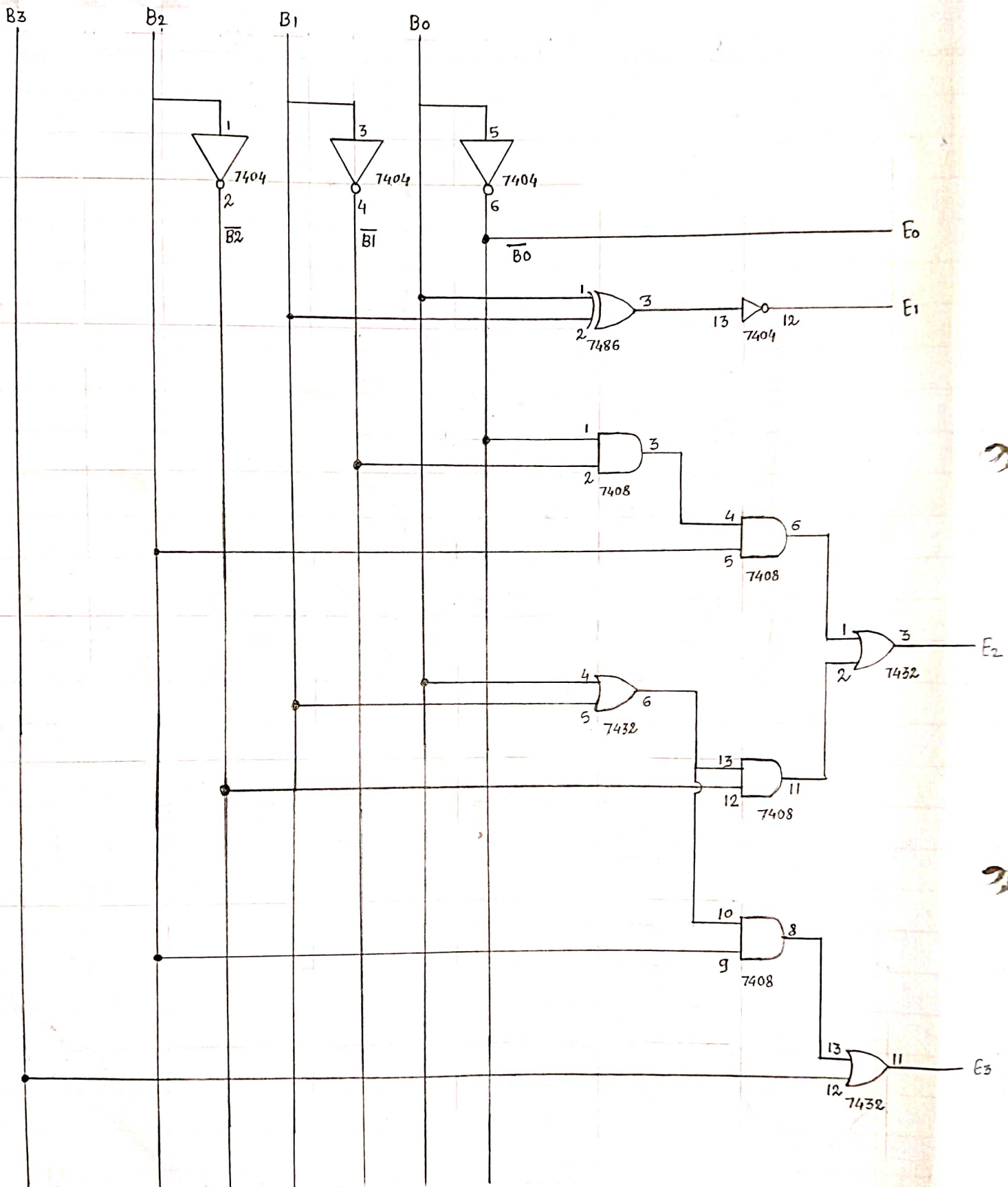


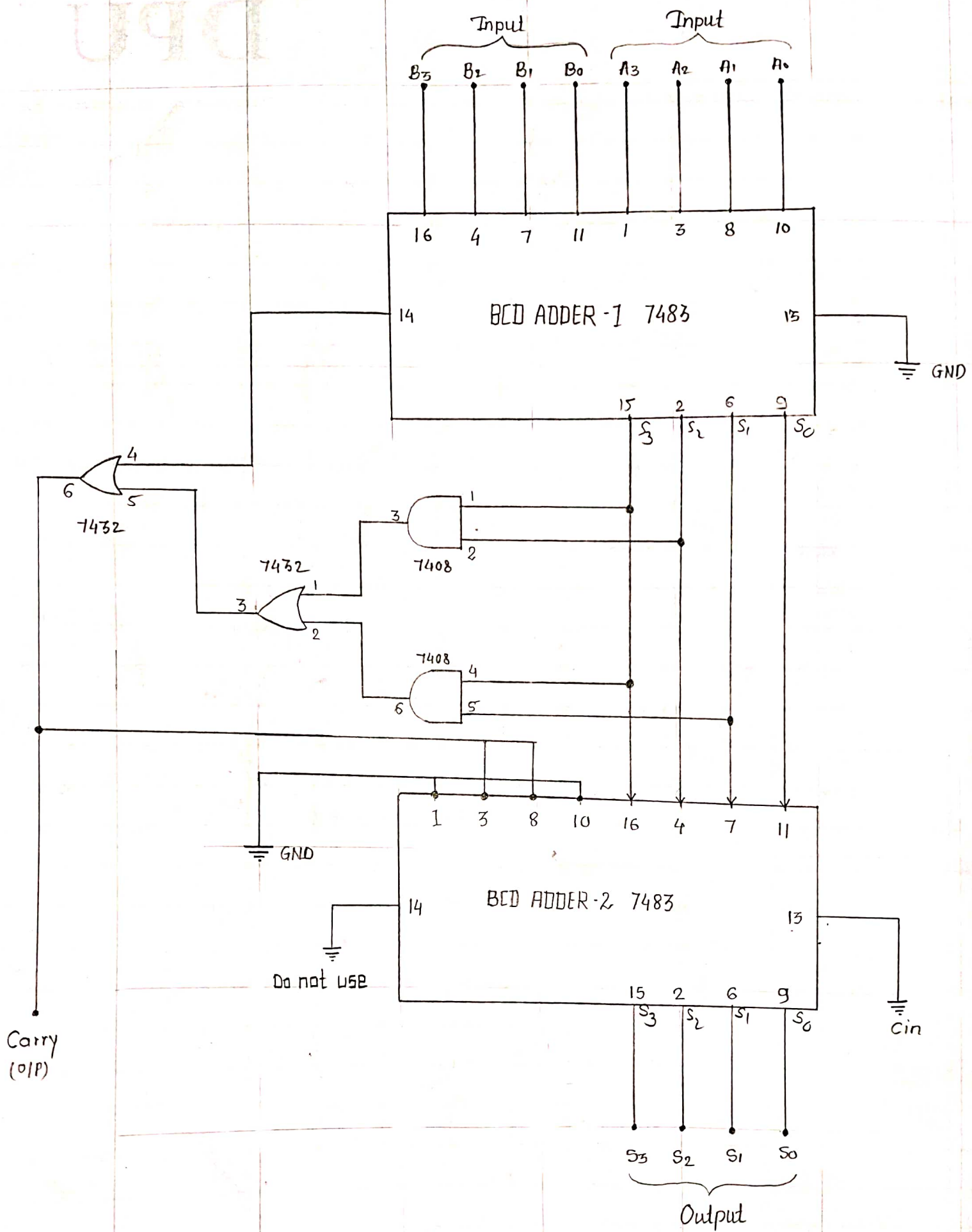


BCD TO EXCESS-3 CONVERTER





BCD ADDER - 7483

Pin Diagram

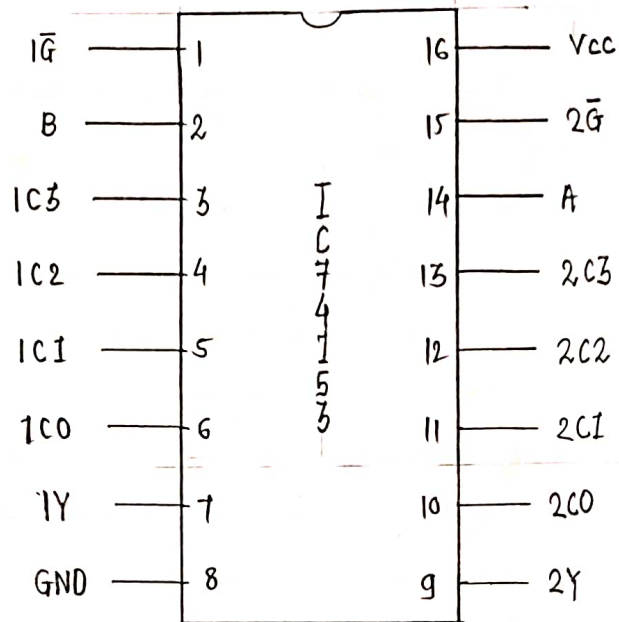


Full Adder Using IC-74153 [Mux]

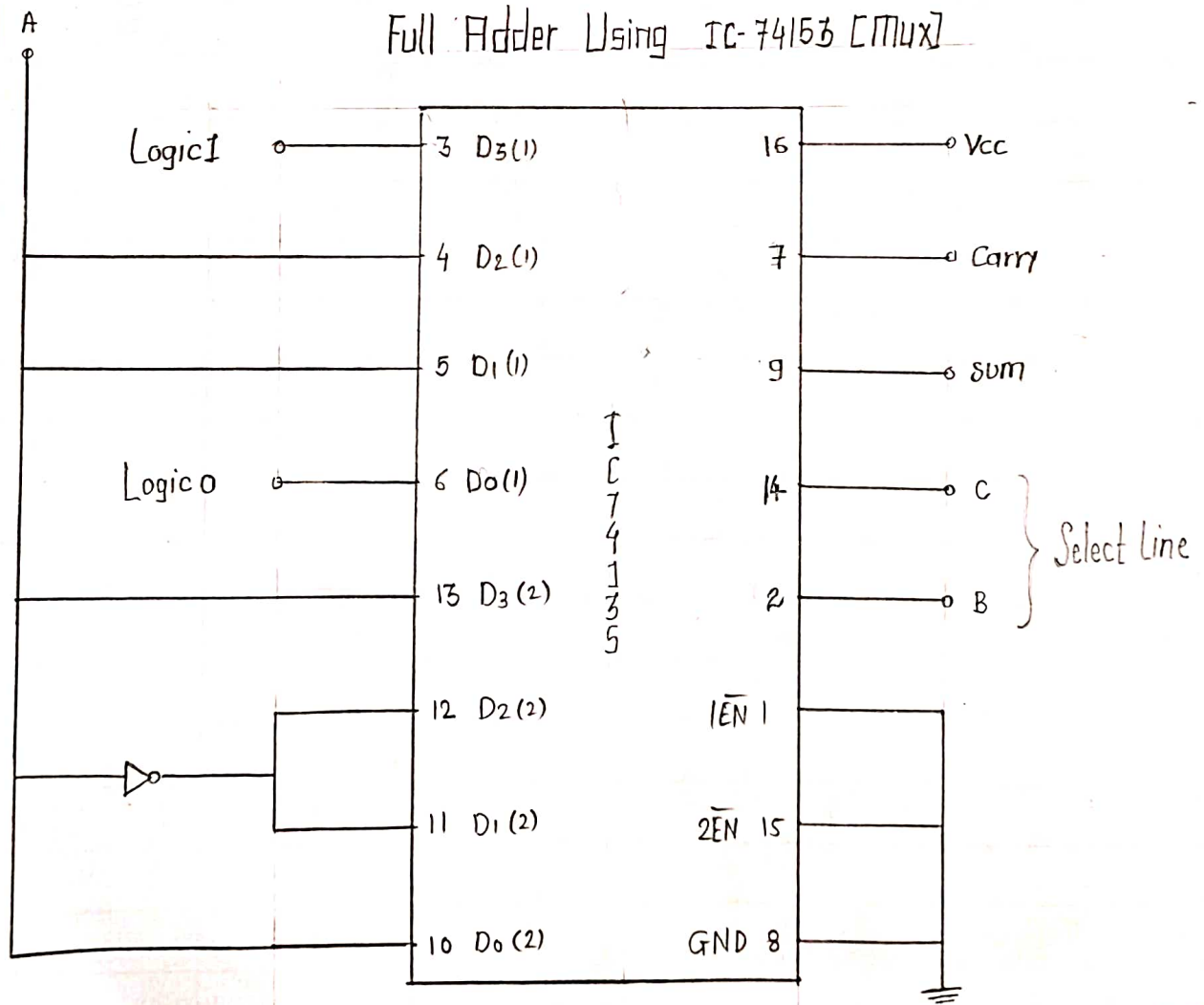


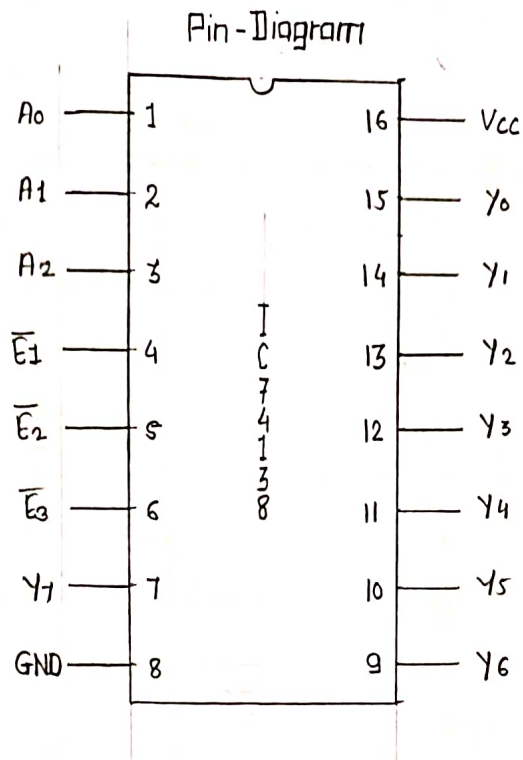


Full Subtractor USING IC-74138 [Decoder]

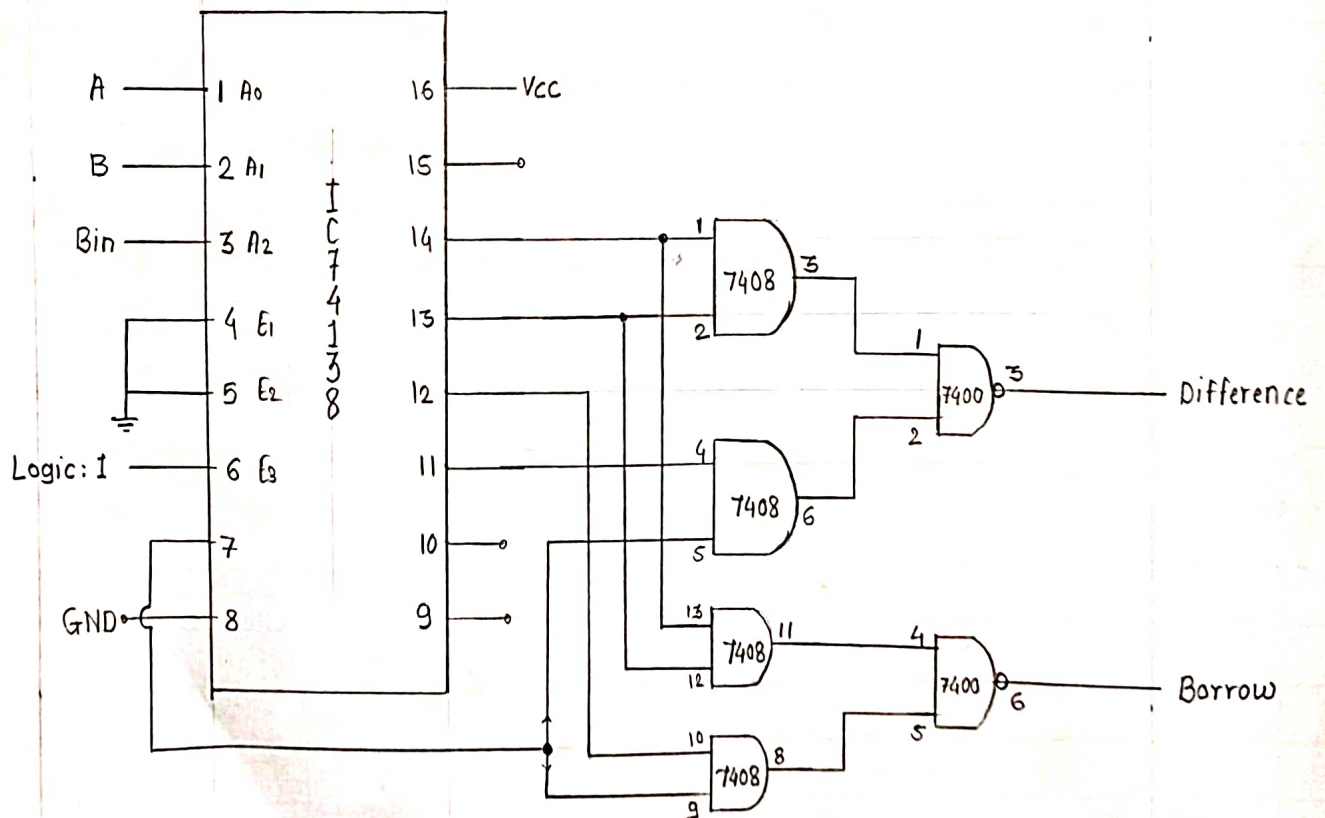


Pin Details

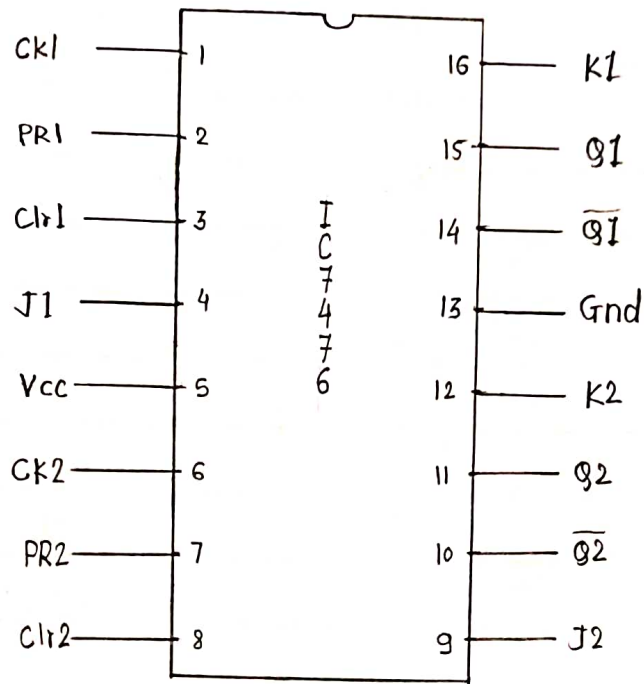


3 bit Asynchronous Up Counter

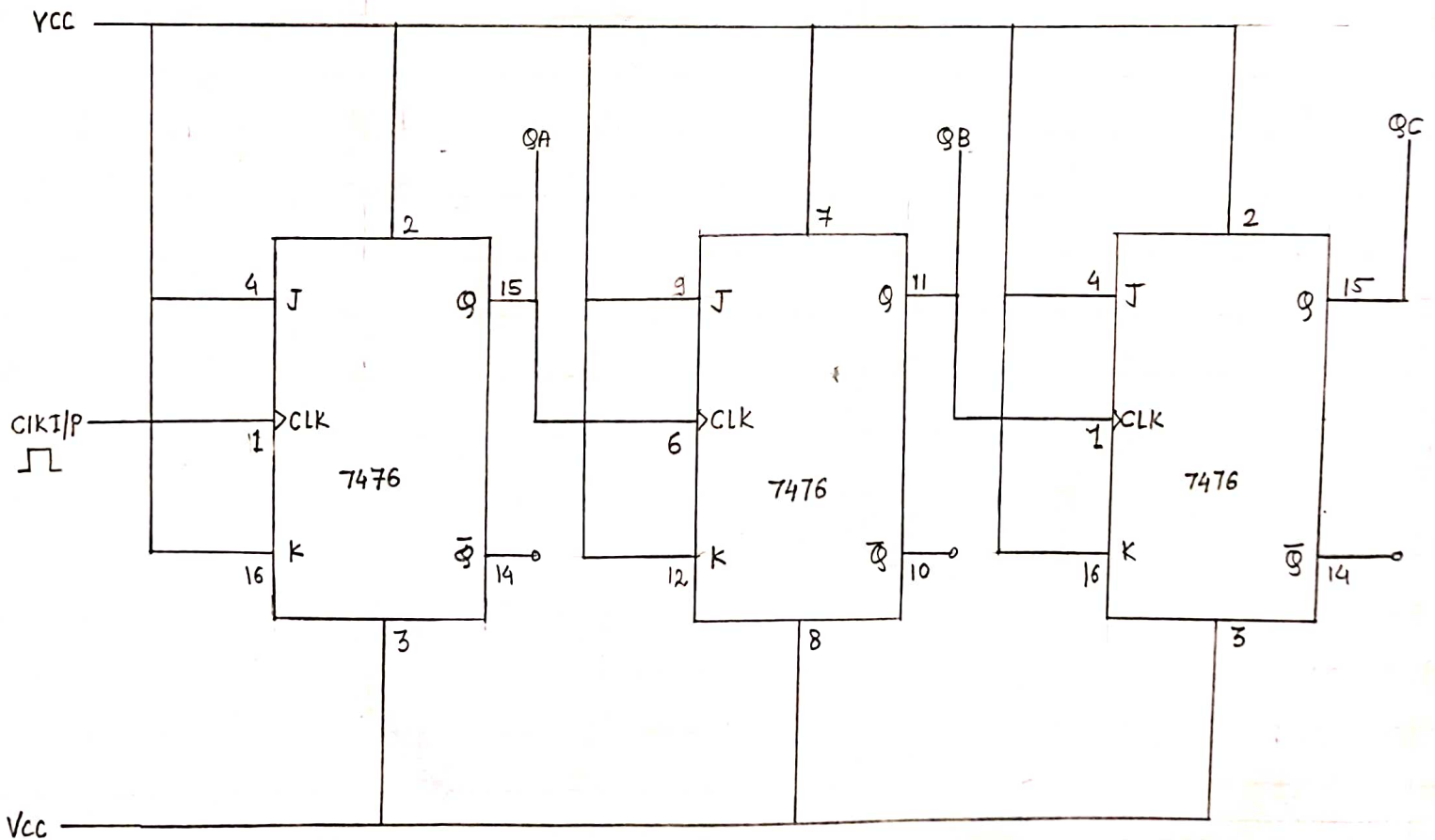

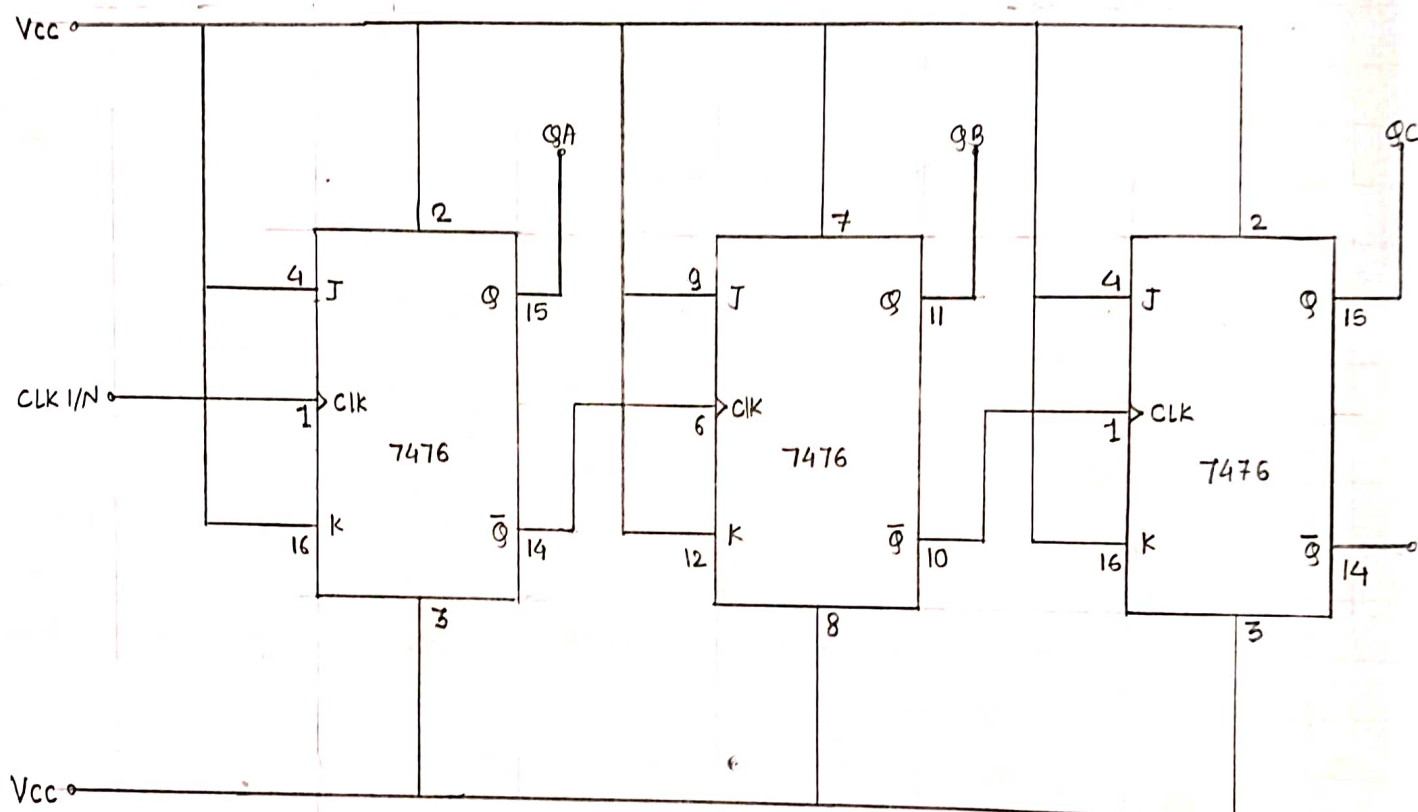


3 bit Asynchronous Down Counter

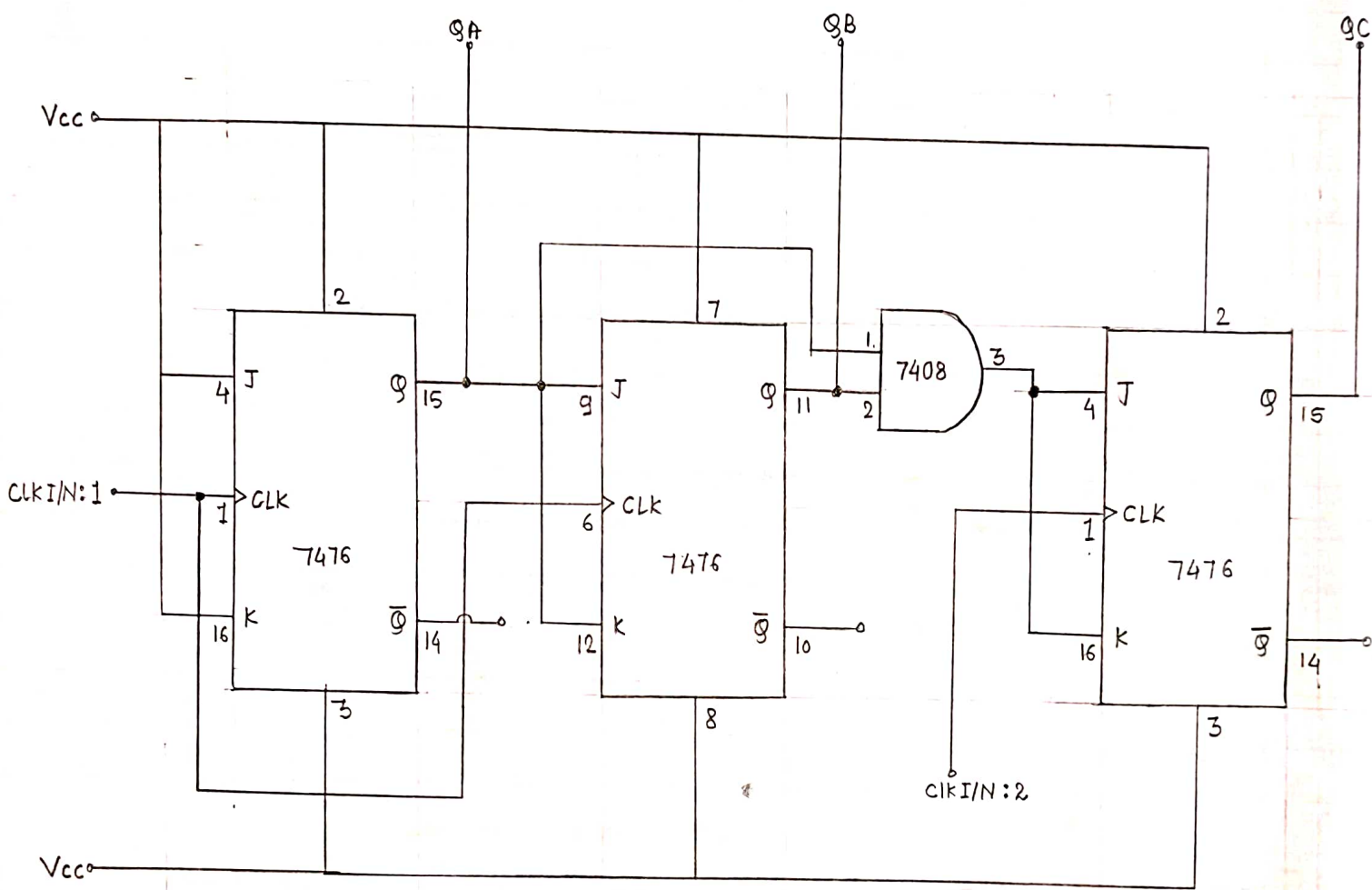


3 bit Synchronous Counter

PIN DIAGRAM

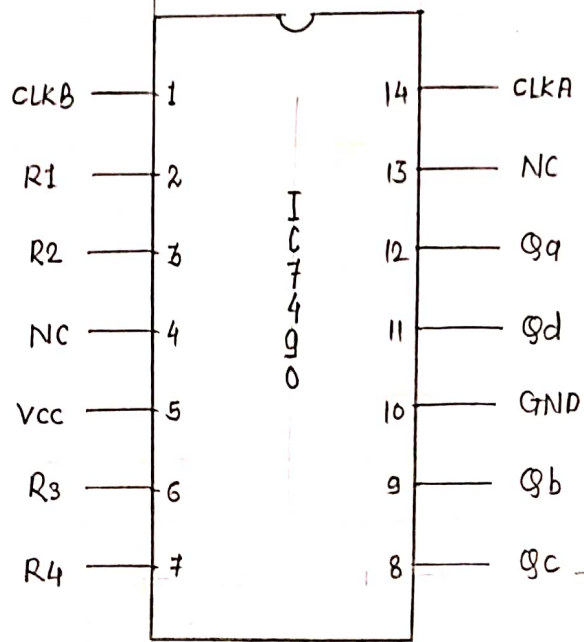


module 'N' Counter Using IC-7490

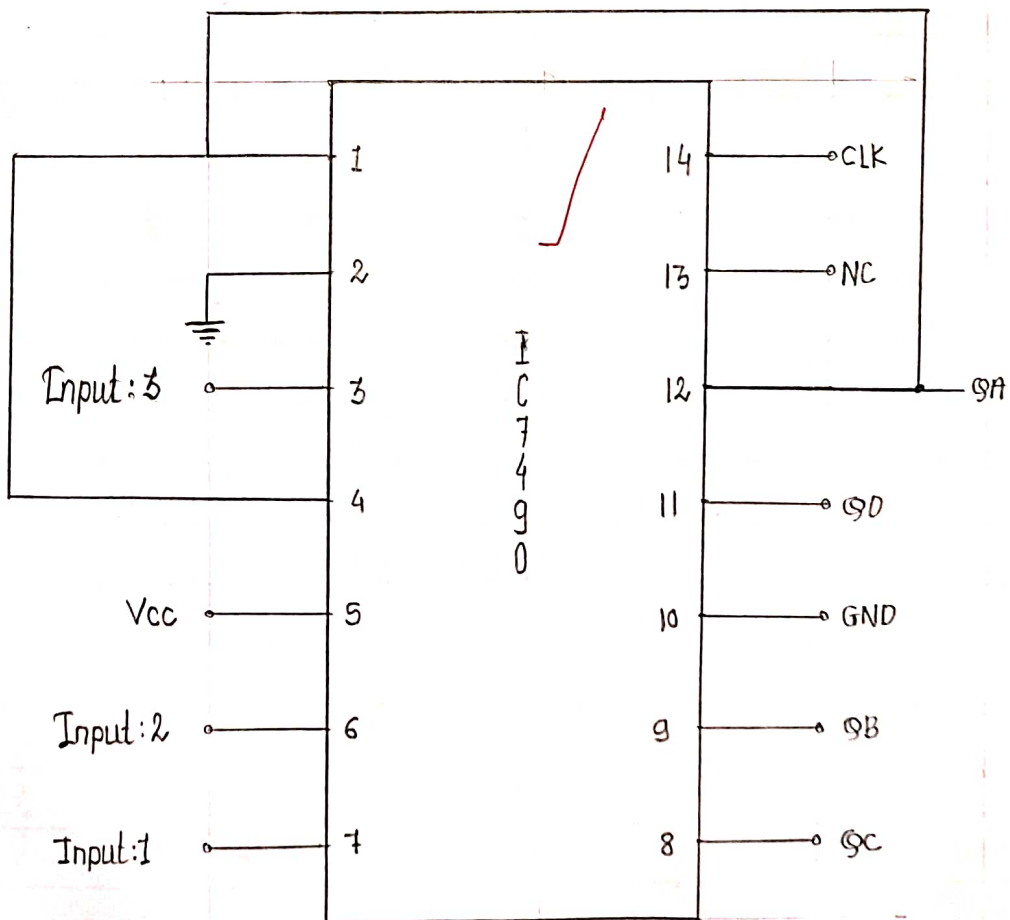



Type here to search

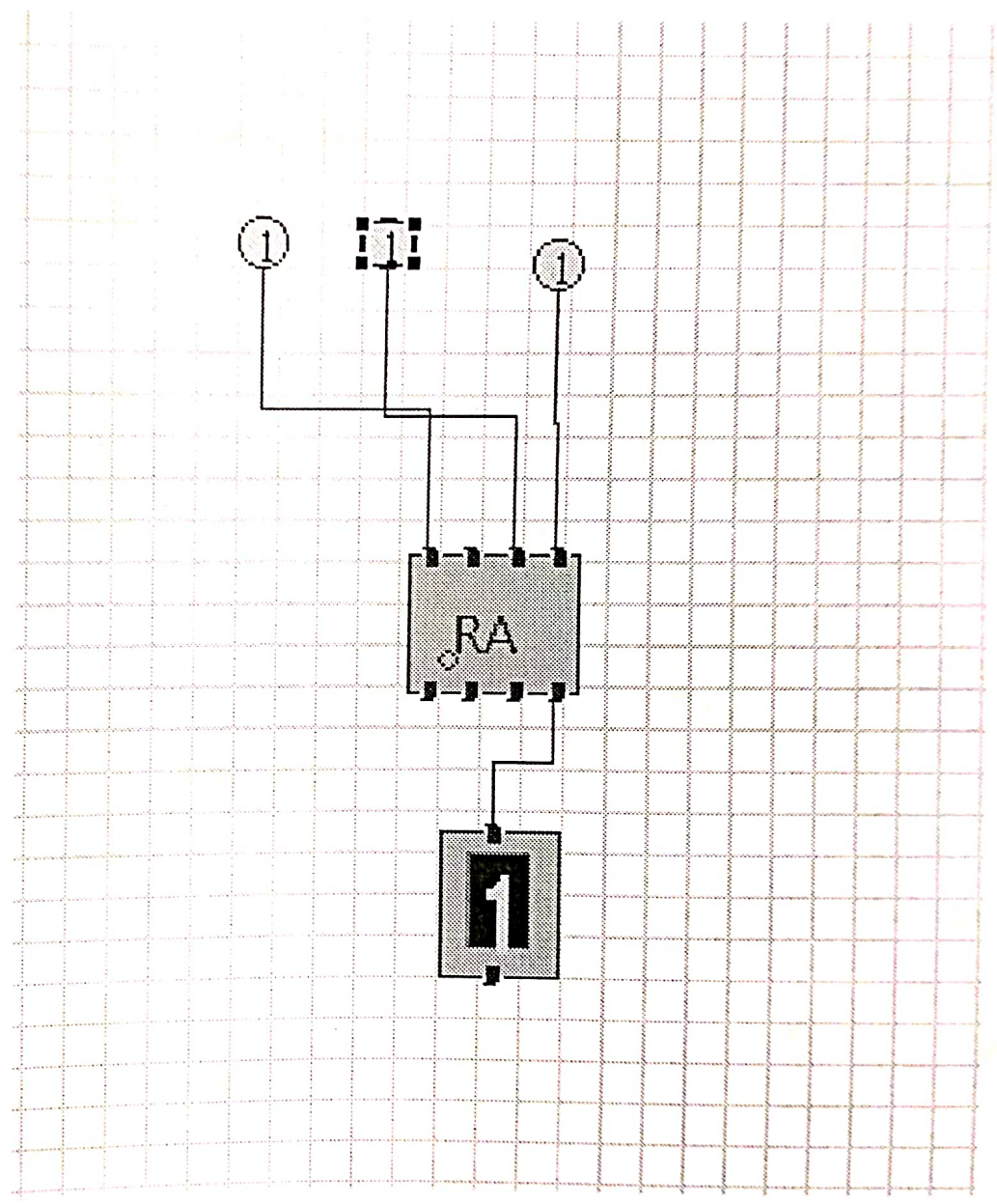

Conclusion: Thus we learned simulation and design of single bit RAMcell.

